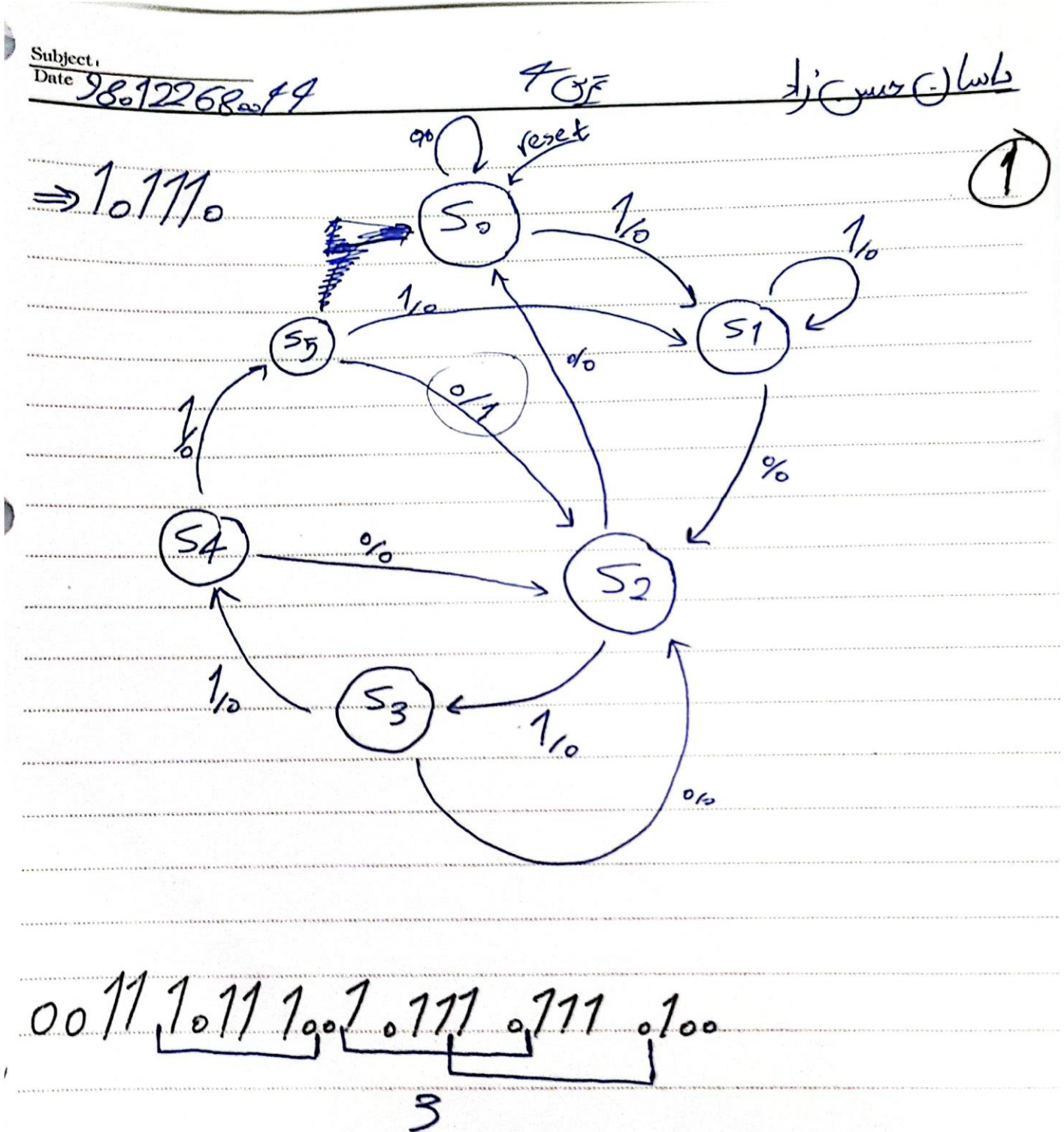


980122680044


ياسان حسن زاد

.1

: sequence detector




## : Tesetbench

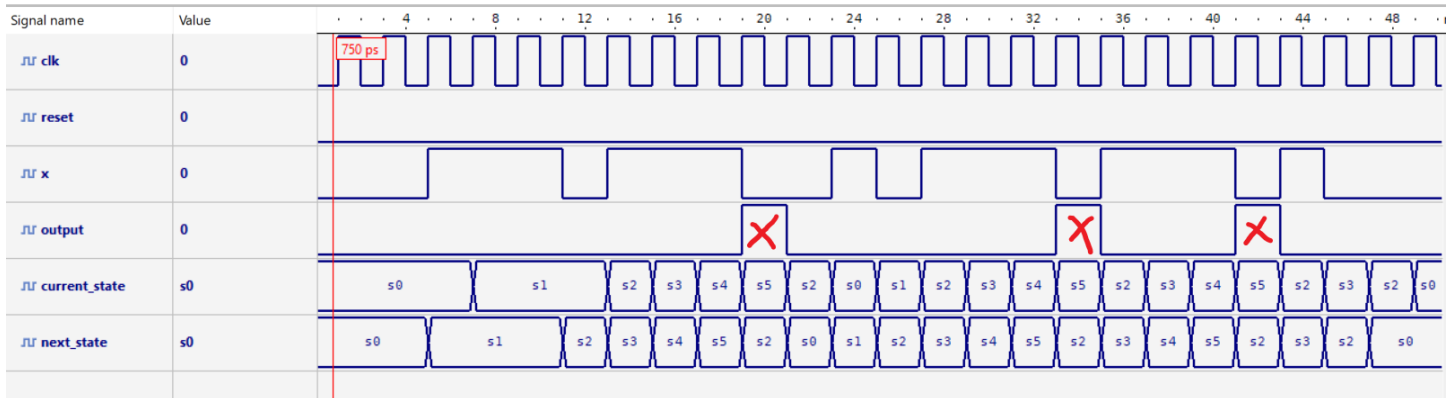

. 2

: sequence detector

 

: Hand Coding

```
architecture T42 of T42 is
  subtype T42_state is std_logic_vector(4 downto 0);
  signal current_state , next_state : T42_state;

  constant s0 : T42_state := "00000";
  constant s1 : T42_state := "00001";
  constant s3 : T42_state := "00011";
  constant s61 : T42_state := "00110";
  constant s62 : T42_state := "10110";
  constant s8 : T42_state := "01000";

begin
```


: REG & CMB & OUTPUT

```
REG : process(clk,reset)
begin
  if reset = '1' then
    current_state <= s0;
  elsif clk'event and clk = '1' then
    current_state <= next_state;
  end if;
end process;

CMB : process(current_state)
begin
  case current_state is
    when s0 => next_state <= s1;
    when s1 => next_state <= s3;
    when s3 => next_state <= s61;
    when s61 => next_state <= s62;
    when s62 => next_state <= s8;
    when s8 => next_state <= s0;
    when others => next_state <= s0;
  end case;
end process;

output <= current_state(3 downto 0);
-- enter your statements here --
```

: Tesetbench

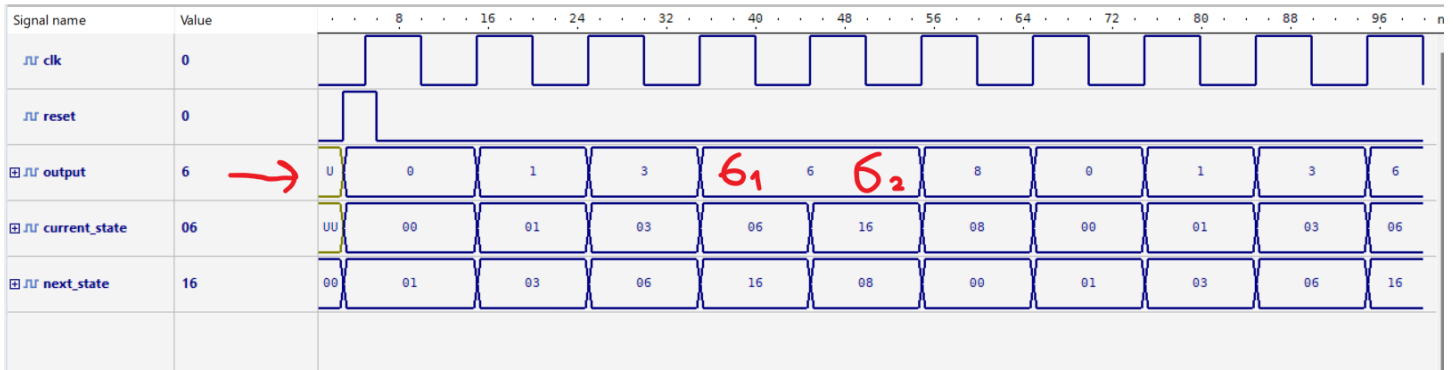


. 3

: sequence detector



Subject: \_\_\_\_\_  
Date \_\_\_\_\_

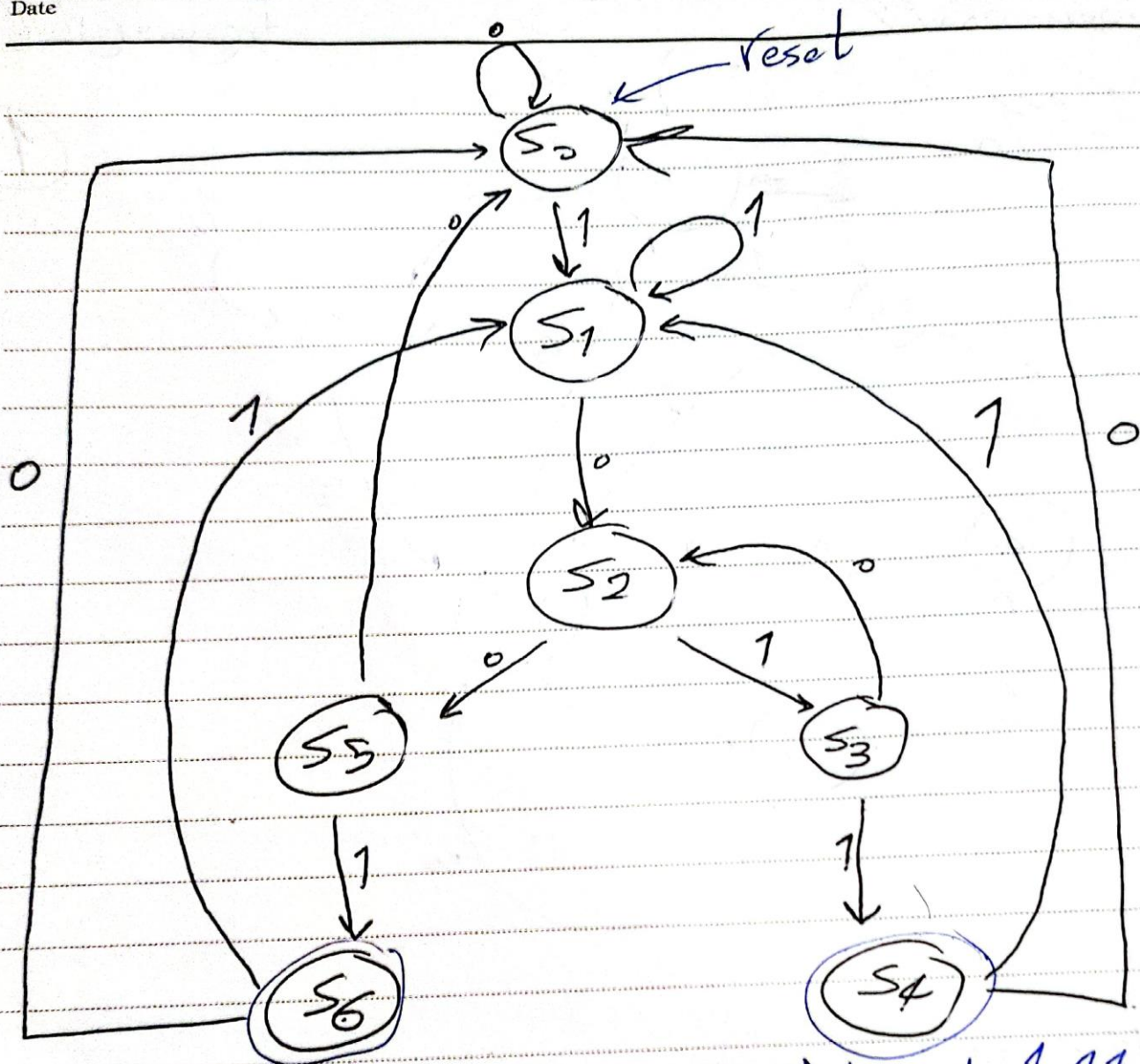

1001 Data in to Reg

Reg to Data out 1011

X = 00 1001 0101 00

## : Datapath & outputs

```

DP_R : process(clk , reset)
begin
    dataout_reg <= (others => 'Z');
    valid_reg <= '0';
    if reset = '1' then
        current_reg <= (others => '0');
        valid <= '0';
    elsif clk'event and clk = '1' then
        if current_state = s6 then
            current_reg <= datain;
        end if;

        if current_state = s4 then
            dataout_reg <= current_reg;
            valid_reg <= '1';
        else
            dataout_reg <= (others => 'Z');
            valid_reg <= '0';
        end if;
    end if;
end process;

dataout <= dataout_reg;
valid <= valid_reg;

```

## : Tesetbench

